

Final

CSEE W3827 - Fundamentals of Computer Systems
Fall 2018

Dec 17, 2018
Prof. Rubenstein

This final contains 4 questions (not counting question 0), totaling 120 points. Question 0 gives an additional 5 points. **BOOKS, NOTES, ELECTRONIC DEVICES ARE NOT PERMITTED!** The time allowed is 3 hours.

Please answer all questions **in the blue book**, using a **separate** page for each question. **Show all work!** We are not just looking for the right answer, but also how you reached the right answer.

QUESTION 0 (5 points off if you don't do this): write your name **CLEARLY**: LAST NAME, FIRST NAME, and UNI on the cover of the blue book and start each of the remaining questions on a new page. If, when sorting the exams according to UNI, yours is sorted incorrectly because of a lack of clarity, you lose the 5 points.

Question 1 involves the game rock-paper-scissors. A brief description of the game is as follows: 2 players play and simultaneously select one of three configurations: (R)ock, (P)aper or (S)cissors. If both players select the same configuration (e.g., both select "rock"), then the game is a (D)raw. If they select different configurations, then there will always be one (W)inner and one (L)oser, with rock beating (smashing) scissors, scissors beating (cutting) paper, and paper beating (covering) rock. The game can be played for multiple rounds, providing hours of entertainment.

1. (30 pts) You are to build a sequential circuit that implements the strategy of one player (who we call the *strategic player*) over multiple rounds. In each round (which takes a clock cycle), the circuit does three things:

- It chooses a configuration (R,P,S) that the strategic player will play for that round
- It reads in a 2-bit input XY that specifies its opponent's configuration (R,P,S) for that round
- It outputs a 2-bit result R_1R_0 that specifies the strategic player's outcome (W,L,D) against the opponent.

The digital representations of the configuration and outcome are specified as:

Opponent Configuration (XY)		Outcome (R_1R_0)	
00	Rock	0X	Draw
01	Paper	10	Lose
10	Scissors	11	Win

(Note for the outcome, the high-order bit R_1 indicates whether someone won the round, and if so, the low order bit then indicates whether the strategic player won).

The configuration played in the $t + 1$ st round (clock cycle) by the strategic player depends on what both players played in the t th round, and on the outcome (W,L,D).

- If the strategic player lost in round t , the configuration in round $t + 1$ matches the configuration in round t .
- If the strategic player wins or draws in round t , the configuration in round $t + 1$ is what would have lost against the opponent in round t .

The following table enumerates the 9 scenarios that the 2 players could have played in the round t , and shows the outcome and what the strategic player will play in round $t + 1$:

Strategic player round t configuration:	R	R	R	P	P	P	S	S	S
Opponent round t config:	R	P	S	R	P	S	R	P	S
Strategic player outcome [(W)in, (L)ose or (D)raw]:	D	L	W	W	D	L	L	W	D
Strategic Player's round $t + 1$ config:	S	R	P	S	R	P	S	R	P


(NOTE: The above is not an example of the game being played over a series of rounds, but shows the outcome and next move for all possible configurations of the current round).

- (20 points) Draw a state machine that implements the sequential circuit described above.
- (10 pts) Give simplified expressions for the sequential circuit using JK flip-flops. For full credit, provide simplified expressions for both output bits and inputs to each of the inputs to the JK flip-flops.

For your reference, the following table excitation table describes the behavior of a JK flip-flop:

$J(t)$	$K(t)$	$Q(t + 1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

 NOTE: Part (a) is 2/3 of the points for this problem, and is a lot less grunt work. Be sure to look at other problems before sinking too much time into part (b).




2. (30 pts) The traditional memory cell (an SR latch with enable) is depicted above on the left, and the manner in which these cells are enabled in a memory chip with 2^k 32-bit words is shown on the figure in the middle (the read and write logic is not shown).

Suppose we wish to design a memory chip, as depicted in the right figure, that takes 2 addresses A_W and A_R such that the chip can simultaneously write data to address A_W while it reads from address A_R .

- (15 pts) Show how to modify the traditional memory cell to implement this functionality (i.e., how would you redraw the left figure?)
- (15 pts) Show how to modify the memory chip's enable circuitry such that you can separately select an address for writing and another for reading (i.e., how would you redraw the middle figure?)

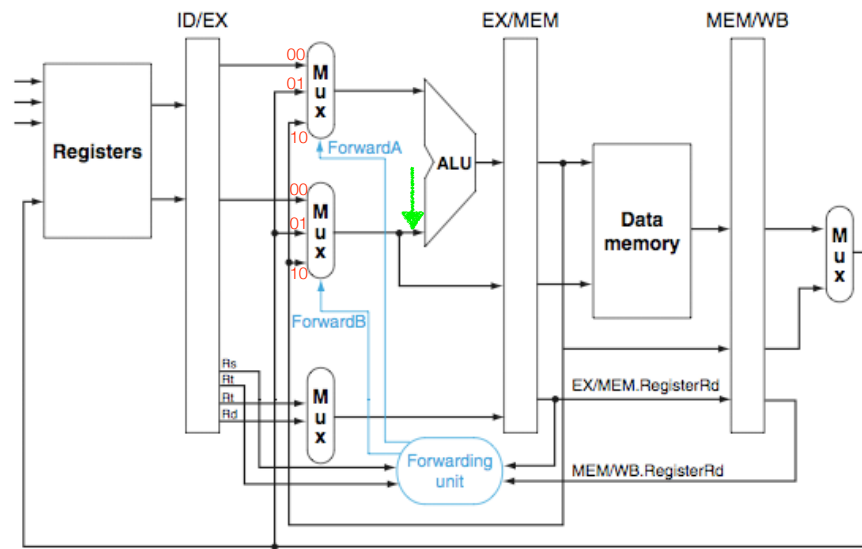You do not need to show the Read or Write Logic. You only need to show the “enable” portion of the memory.



4. (30 pts) The above figure shows a portion of the pipeline architecture with data-forwarding implemented. The green arrow points to a region where a MUX that allows one to select between the second register value and a constant exists (it was the same location as it would be in the single-cycle architecture).

Consider the following snippet of code:

```
add $s0, $zero, $zero
addi $s1, $zero, 40000
lw $s0, 0($s1)
sw $s0, 1000($s1)
```

and suppose that the value stored in memory at address 40000 equals 100.

Suppose the designer figures that because data forwarding is implemented, he/she doesn't need to stall any of the above instructions when running them through the pipeline.

- (10 pts) What registers and/or memory locations will have incorrect values stored as a result of not implementing the stall, and what (incorrect) value could occur? Explain in 1 sentence how that particular value occurred instead of the correct value.
- (10 pts) It is possible to add additional forwarding logic such that a stall would not be necessary. Indicate where and how. Either draw a picture of the circuitry where a change is being made, or simply provide a short, clear description of the change.
- (10 pts) Does the above change in part (b) prevent all stalls due to data dependencies? If so, give a short, 1 sentence explanation as to why. If not, give an example MIPS code snippet that would still require a stall due to a data dependence.

You have reached the end of the exam. Have a great Winter Break!