

# CSEE 3827: Fundamentals of Computer Systems, Spring 2022

## Lecture 3

Prof. Dan Rubenstein ([danr@cs.columbia.edu](mailto:danr@cs.columbia.edu))

# Agenda (M&K 2.3-2.5)

---

- Standard Forms
  - Product-of-Sums (PoS)
  - Sum-of-Products (SoP)
    - converting between
  - Min-terms and Max-terms
- Simplification via Karnaugh Maps (K-maps)
  - 2, 3, and 4 variable
  - Implicants, Prime Implicants, Essential Prime Implicants
  - Using K-maps to reduce
  - PoS form
  - Don't Care Conditions

# Standard Forms

---

- There are many ways to express a boolean expression

$$\begin{aligned} F &= XYZ + XYZ + XZ \\ &= XY(Z + Z) + XZ \\ &= XZ \end{aligned}$$

- It is useful to have a standard or canonical way
- Derived from truth table
- Generally not the simplest (fewest literals) form

# Two principle standard forms

---

- Sum-of-products (SoP)
- Product-of-sums (PoS)
- We will deal mostly in this course with SoP

# Product and sum terms


---

- Product term: logical AND of literals (e.g.,  $X\bar{Y}Z$ )
- Sum term: logical OR of literals (e.g.,  $A + \bar{B} + C$ )


# PoS & SoP

---

- Sum of products (SoP): OR of ANDs (OR of product terms)

$$\text{e.g., } F = \bar{Y} + \bar{X}Y\bar{Z} + XY$$


- Product of sums (PoS): AND of ORs (AND of sum terms)

$$\text{e.g., } G = X(\bar{Y} + Z)(X + Y + \bar{Z})$$


# PoS and SoP not always simplest form

---

- e.g.,  $F = ABD + ABE + C(D+E)$ 
  - $(AB+C)(D+E)$  is **simplest** (fewest literals) form (5 literals)
    - know it's simplest because each literal appears only once
  - simplest SoP form:  $ABD + ABE + CD + CE$  (10 literals)
  - simplest PoS form:  $(A+C)(B+C)(D+E)$  is (6 literals)

# Converting any expression to SoP

---

- Just “multiply” through and simplify

•e.g.,  $G = X(Y + Z)(X + Y + Z)$

•  $= XYX + XYY + XYZ + XZX + XZY + XZZ$  and then simplify

•  $= XY + XY + XYZ + XZ + XZY + XZ$  (removed duplicate literals in prod. term)

•  $= XY + XZ$  (removed repeated prod. terms)



# Converting from SoP to PoS

---

- Complement, multiply through, complement (swap + and  $\cdot$  ops, flip literals)

- e.g.,  $F = \bar{Y}\bar{Z} + \bar{X}\bar{Y}Z + X\bar{Y}\bar{Z}$

swap ops, flip literals

- $\bar{F} = (Y+Z)(\bar{X} + Y + \bar{Z})(\bar{X} + \bar{Y} + Z)$

simplify  $\bar{F}$

- $= YZ + \bar{X}Y + \bar{X}\bar{Z}$  (after lots of simplifying)

swap ops, flip literals

- $F = (\bar{Y}+\bar{Z})(X+\bar{Y})(X+\bar{Z})$

- Why did this work?

- Since  $\bar{F} = YZ + \bar{X}Y + \bar{X}\bar{Z}$  in SoP form

- Complementing  $\bar{F}$  in SoP form yields  $F$  in PoS form

# Minterms and Maxterms

# Minterms

e.g., Minterms for 3 variables A,B,C


A	B	C	minterm
0	0	0	m0 $\bar{A}\bar{B}\bar{C}$
0	0	1	m1 $\bar{A}\bar{B}C$
0	1	0	m2 $\bar{A}B\bar{C}$
0	1	1	m3 $\bar{A}BC$
1	0	0	m4 $A\bar{B}\bar{C}$
1	0	1	m5 $A\bar{B}C$
1	1	0	m6 $AB\bar{C}$
1	1	1	m7 $ABC$

$2^3$

- A product term in which all variables appear exactly once, either complemented or uncomplemented.
- Each minterm evaluates to 1 for **exactly one** assignment of values to all variables (one row in truth table), 0 for all others.
- e.g., for what values of A,B,C does  $\bar{A}\bar{B}\bar{C}$  evaluate to 1?

Handwritten diagram illustrating the evaluation of the minterm  $\bar{A}\bar{B}\bar{C}$  for the assignment A=0, B=0, C=0. The variables A, B, and C are shown in boxes. The expression  $\bar{A}\bar{B}\bar{C}$  is written above the boxes. The values 0, 0, 0 are written above the boxes. The expression  $\sum(m_0, m_1, m_3, m_4) = 1$  is written below the boxes, with a note "BC" under the sum.

# Minterms

 

e.g., Minterms for 3 variables A,B,C

A	B	C	minterm
0	0	0	m0 $\bar{A}\bar{B}\bar{C}$
0	0	1	m1 $\bar{A}\bar{B}C$
0	1	0	m2 $\bar{A}B\bar{C}$
0	1	1	m3 $\bar{A}BC$
1	0	0	m4 $A\bar{B}\bar{C}$
1	0	1	m5 $A\bar{B}C$
1	1	0	m6 $AB\bar{C}$
1	1	1	m7 $ABC$

- A product term in which all variables appear exactly once, either complemented or uncomplemented.
- Each minterm evaluates to 1 for **exactly one** assignment of values to all variables (one row in truth table), 0 for all others.
- e.g., for what values of A,B,C does  $\bar{A}\bar{B}C$  evaluate to 1?
- Ans: A=0, B=0, C=1 (that's the only one)

# Minterms

---

e.g., Minterms for 3 variables A,B,C

A	B	C	minterm
0	0	0	m0 $\bar{A}\bar{B}\bar{C}$
0	0	1	m1 $\bar{A}\bar{B}C$
0	1	0	m2 $\bar{A}B\bar{C}$
0	1	1	m3 $\bar{A}BC$
1	0	0	m4 $A\bar{B}\bar{C}$
1	0	1	m5 $A\bar{B}C$
1	1	0	m6 $AB\bar{C}$
1	1	1	m7 $ABC$

- A product term in which all variables appear exactly once, either complemented or uncomplemented.
- Each minterm evaluates to 1 for **exactly one** assignment of values to all variables (one row in truth table), 0 for all others.
- Each product term denoted by  $mX$  where X corresponds to the row of the truth table where variable value assignments cause that minterm to equal 1.

# Minterm examples (with 3 variables, A,B,C)

---

- ABC is a minterm, and is true when and only when  $A=1, B=1, C=1$
- $\overline{A}BC$  is a minterm and is true when and only when  $A=0, B=1, C=0$
- A function can be described as a **sum of its minterms**

• e.g.,  $F = B(A \oplus \overline{C}) = B(AC + \overline{A}\overline{C}) = \underbrace{ABC + \overline{A}BC}_{\text{minterms}}$

- $F=1$  when ABC is true OR  $\overline{A}BC$  is true
  - i.e.,  $F = 1$  when  $A=1 \ \& \ B=1 \ \& \ C=1$  OR when  $A=0 \ \& \ B=1 \ \& \ C=0$
- $F = 0$  otherwise

## A few more Minterm examples (of 3 variables A,B,C)

---


- $G(A,B,C) = BC$  (G's value is independent of A)
  - $G = ABC + \overline{A}BC$  (G is defined over A,B,C, minterms contain all vars)
  - $G = 1$  when & only when  $A=1, B=1, C=1$  OR  $A=0, B=1, C=1$
- $H(A,B,C) = A$ 
  - $H = ABC + AB\overline{C} + A\overline{B}C + A\overline{B}\overline{C}$  (all combos of B,C when  $A=1$ )
- $F = A + BC$ 
  - $= H + G = \underbrace{A\overline{B}\overline{C} + A\overline{B}C + A\overline{B}\overline{C} + ABC}_{A} + \underbrace{\overline{A}BC}_{BC}$  (note minterm ABC repeated)

# Minterms to describe a function

- sometimes also called a **minterm expansion: OR (SUM) appropriate minterms together**

This “term” is TRUE when A=0,B=1,C=0

Hence F=1 when A=0,B=1,C=0

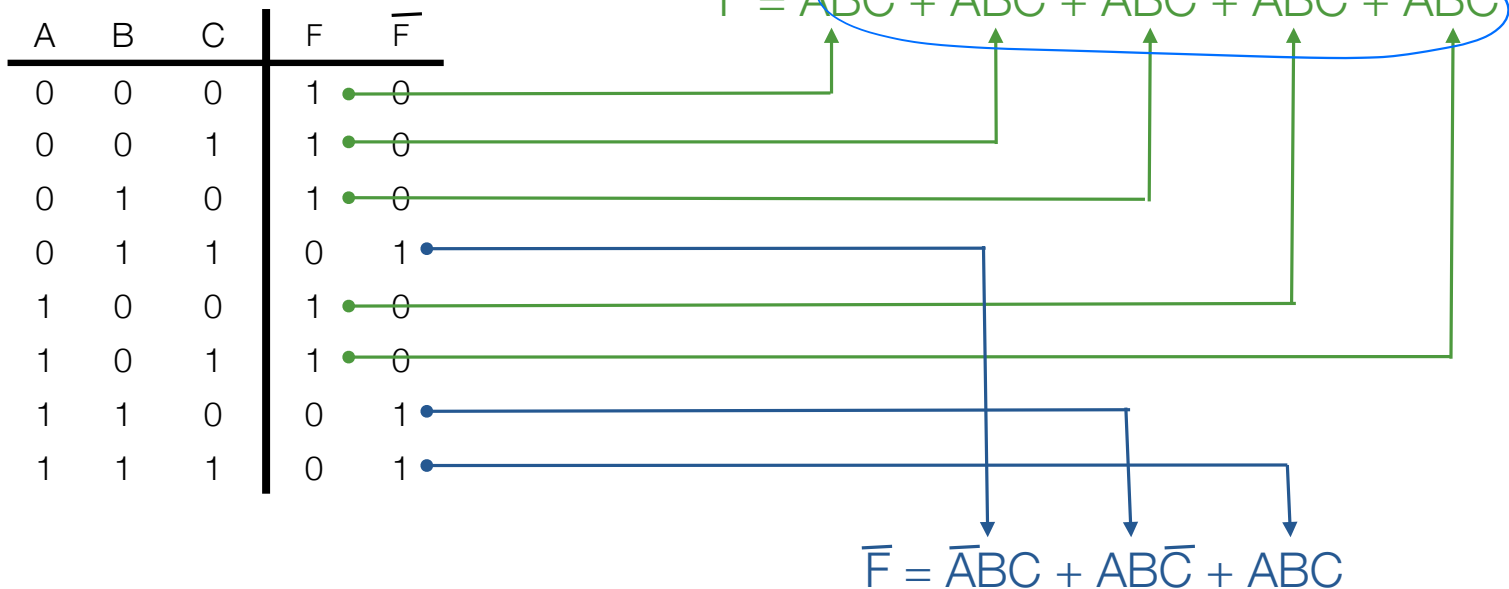

Function and its complement function use all midterms, share none in common



# Sum of minterms form

---

- The logical OR of all minterms for which  $F = 1$ .

A	B	C	minterm	F
0	0	0	m0 $\bar{A}\bar{B}\bar{C}$	0
0	0	1	m1 $\bar{A}\bar{B}C$	1
0	1	0	m2 $\bar{A}B\bar{C}$	1
0	1	1	m3 $\bar{A}BC$	1
1	0	0	m4 $A\bar{B}\bar{C}$	0
1	0	1	m5 $A\bar{B}C$	0
1	1	0	m6 $AB\bar{C}$	0
1	1	1	m7 $ABC$	0

$$\begin{aligned}F &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC \\&= m1 + m2 + m3 \\&= \underline{\underline{\sum m(1,2,3)}}$$

# Minterm form cont'd


*(variables appear once in each minterm)*

A	B	C	F	$\overline{F}$	minterm
0	0	0	1	0	m0 $\overline{A}\overline{B}\overline{C}$
0	0	1	1	0	m1 $\overline{A}\overline{B}C$
0	1	0	1	0	m2 $\overline{A}B\overline{C}$
0	1	1	0	1	m3 $\overline{A}BC$
1	0	0	1	0	m4 $A\overline{B}\overline{C}$
1	0	1	1	0	m5 $A\overline{B}C$
1	1	0	0	1	m6 $AB\overline{C}$
1	1	1	0	1	m7 $ABC$

$$\begin{aligned}
 F &= \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + A\overline{B}C \\
 &= m0 + m1 + m2 + m4 + m5 \\
 &= \sum m(0,1,2,4,5)
 \end{aligned}$$

$$\begin{aligned}
 \overline{F} &= \overline{A}BC + AB\overline{C} + ABC \\
 &= m3 + m6 + m7 \\
 &= \sum m(3,6,7)
 \end{aligned}$$

# Minterms as a circuit

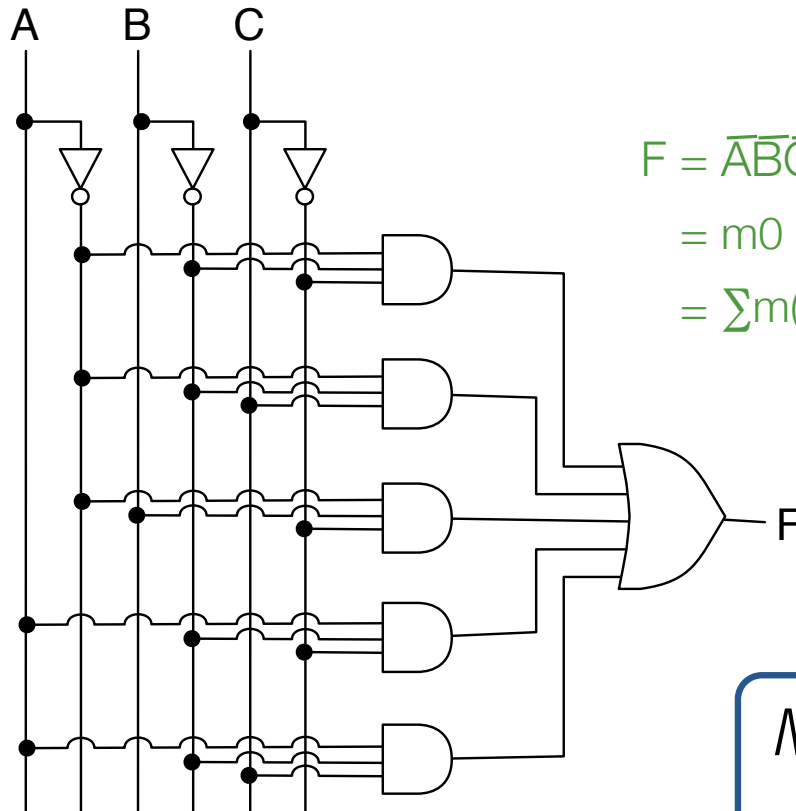

$$\begin{aligned} F &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C \\ &= m_0 + m_1 + m_2 + m_4 + m_5 \\ &= \sum m(0,1,2,4,5) \end{aligned}$$

*Minterm form is not  
simplified form!*

# Simplest Form v. SoP Form v. Minterm Form

---

- Can be the same, but not always
- e.g.,  $F = WX(Y+Z)$  (note 4 variables)
  - SoP form:  $WXY + WXZ$
  - Minterm form:  $WXYZ + WXY\bar{Z} + WX\bar{Y}Z$
- e.g.,  $F = WX(\bar{Y}\bar{Z} + \bar{Y}Z)$ 
  - SoP form:  $WX\bar{Y}\bar{Z} + WX\bar{Y}Z$
  - Minterm form:  $WX\bar{Y}\bar{Z} + WX\bar{Y}Z$

# Maxterms - “Dual” of minterms

---

A	B	C	maxterm
0	0	0	M0 $A+B+C$
0	0	1	M1 $A+B+\bar{C}$
0	1	0	M2 $A+\bar{B}+C$
0	1	1	M3 $A+\bar{B}+\bar{C}$
1	0	0	M4 $\bar{A}+B+C$
1	0	1	M5 $\bar{A}+B+\bar{C}$
1	1	0	M6 $\bar{A}+\bar{B}+C$
1	1	1	M7 $\bar{A}+\bar{B}+\bar{C}$

- A sum term in which all variables appear once, either complemented or uncomplemented.
- Each maxterm evaluates to 0 for exactly one variable assignment, 1 for all others.
- Denoted by MX where X corresponds to the variable assignment for which  $MX = 0$ .

# Maxterms: not as intuitive as minterms

---

- $F = \bar{A}\bar{C} + \bar{B}$ 
  - turns out  $F = 1$  when  $(A=1 \text{ or } B=0 \text{ or } C=0)$  AND  $(A=0 \text{ or } B=0 \text{ or } C=1)$  AND  $(A=0 \text{ or } B=0 \text{ or } C=0)$ ,
  - i.e.,  $F = (A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})$
- Think of it as forcing  $F$  to 0 when  $F$  doesn't equal a maxterm
  - e.g.,  $F = 0$  when  $A=1, B=1, C=1$ .
  - In other words, for  $F=1$ , it is necessary (but not sufficient) that either  $A=0$  OR  $B=0$  OR  $C=0$ , i.e.,  $(A+B+C = 1)$  AND some other conditions
  - Thus, the maxterm  $(\bar{A}+\bar{B}+\bar{C})$  is included in the sum for  $F$

# Maxterm description of a function

- sometimes also called **conjunctive normal form (CNF)**
- sometimes also called a **maxterm expansion**

This “term” is FALSE when  
 $A=1 \ \& \ B=1 \ \& \ C=0$

A	B	C	F	$\overline{F}$
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

$$F = (A + \overline{B} + \overline{C}) (\overline{A} + \overline{B} + C) (\overline{A} + \overline{B} + \overline{C})$$

Force to 0

When inputs “satisfy” a Maxterm, the function equals 0

# Product of maxterms form

---

- The logical AND of all maxterms for which  $F = 0$ .

A	B	C	maxterm	F
0	0	0	M0 $A+B+C$	0
0	0	1	M1 $A+B+\bar{C}$	1
0	1	0	M2 $A+\bar{B}+C$	1
0	1	1	M3 $A+\bar{B}+\bar{C}$	1
1	0	0	M4 $\bar{A}+B+C$	0
1	0	1	M5 $\bar{A}+B+\bar{C}$	0
1	1	0	M6 $\bar{A}+\bar{B}+C$	0
1	1	1	M7 $\bar{A}+\bar{B}+\bar{C}$	0

$$\begin{aligned} F &= (A+B+C) (\bar{A}+B+C) (\bar{A}+B+\bar{C}) (\bar{A}+\bar{B}+C) (\bar{A}+\bar{B}+\bar{C}) \\ &= (M0) (M4) (M5) (M6) (M7) \\ &= \prod M(0,4,5,6,7) \end{aligned}$$



# Summary of Minterms and Maxterms

---

	F	$\bar{F}$
Minterms (SOP)	$\sum m(F = 1)$	$\sum m(F = 0)$
Maxterms (POS)	$\prod M(F = 0)$	$\prod M(F = 1)$

# One final example

---

A	B	C	F	$\overline{F}$
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

	F	$\overline{F}$
Minterms (SOP)		
Maxterms (POS)		

# Standard Form Example

---

A	B	C	F	$\overline{F}$	m/M
0	0	0	0	1	0
0	0	1	1	0	1
0	1	0	0	1	2
0	1	1	1	0	3
1	0	0	0	1	4
1	0	1	1	0	5
1	1	0	1	0	6
1	1	1	0	1	7

F

$\overline{F}$

Sum of products  
(SOP)

$\Sigma m(1,3,5,6)$

$\Sigma m(0,2,4,7)$

Product of sums  
(POS)


$\Pi M(0,2,4,7)$

$\Pi M(1,3,5,6)$

# Converting between canonical forms

---

	F	$\bar{F}$
Minterms (SOP)	$\sum m(F = 1)$	$\sum m(F = 0)$
Maxterms (POS)	$\prod M(F = 0)$	$\prod M(F = 1)$

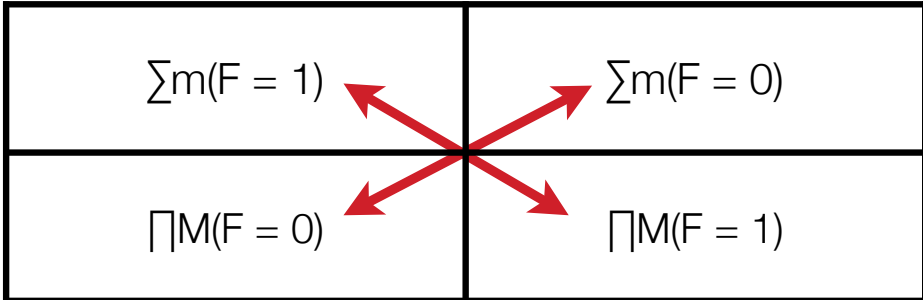

**DeMorgans: same terms**

$$\overline{\sum m(F = 1)} = \prod M(F = 1)$$

# Simplification Methods

# Simplification Example

---

- Simplify  $F = XY + X\bar{Y} + \bar{X}Y$

X	Y	F	m
0	0	0	$\bar{X}\bar{Y}$
0	1	1	$\bar{X}Y$
1	0	1	$X\bar{Y}$
1	1	1	$XY$

- $F = X(Y + \bar{Y}) + \bar{X}Y = X + \bar{X}Y$
- Can this be simplified further?

# Simplification example cont'd

- $F = X + \bar{X}Y$
- Note important identity:  $X + XY = X$  or...  $X = X + XY$ 
  - e.g.,  $X$ =female,  $Y$  = red hair: Say “yes” if  $X$  (you are female) or  $XY$  (you are female and have red hair) - it's enough just ask if female
- so  $F = X + \bar{X}Y = (X + \bar{X}Y) + XY = X + \bar{X}Y + XY = X + (\bar{X} + X)Y = X + Y$
- so most simplified,  $F = X + Y$   
(just ask if female or have red hair)

The point: simplification not  
always so easy / obvious  
Additional tools are needed!

X	Y	F	m
0	0	0	$\bar{X}\bar{Y}$
0	1	1	$\bar{X}Y$
1	0	1	$X\bar{Y}$
1	1	1	$XY$

# Karnaugh Maps



# Karnaugh Maps (K-Maps)

---

- K-maps are a nice structure to help simplify functions in sum-of-product form (or product-of-sums form)
  - Gets functions simplified to either SoP or PoS form which is not necessarily absolute simplest, but it's good enough (for this course)
- We will use it to simplify functions to SoP form with up to 4 variables

# Karnaugh maps (a.k.a., K-maps)

---

- All functions can be expressed with a K-map
- There is one square in the map for each minterm in a function's truth table

X	Y	F
0	0	m0
0	1	m1
1	0	m2
1	1	m3

		Y	
X		0	1
	0	m0 $\overline{X}\overline{Y}$	m1 $\overline{X}Y$
	1	m2 $X\overline{Y}$	m3 $XY$

A K-map is just a 2-dimensional way of representing the function in a truth table

# Karnaugh maps

- All functions can be expressed with a map
- There is one square in the map for each minterm in a function's truth table

X	Y	F
0	0	m0
0	1	m1
1	0	m2
1	1	m3

		Y	
X		0	1
0		m0 $\overline{X}\overline{Y}$	m1 $\overline{X}Y$
1		m2 $X\overline{Y}$	m3 $XY$

$X=0$  ( $\overline{X}$ )


$X=1$  ( $X$ )

A K-map is just a 2-dimensional way of representing the function in a truth table

# Karnaugh maps

- All functions can be expressed with a map
- There is one square in the map for each minterm in a function's truth table


X	Y	F
0	0	m0
0	1	m1
1	0	m2
1	1	m3

 
 
# Karnaugh maps express functions


---

- Fill out table with value of a function



 
# Karnaugh maps express functions

- Fill out table with value of a function


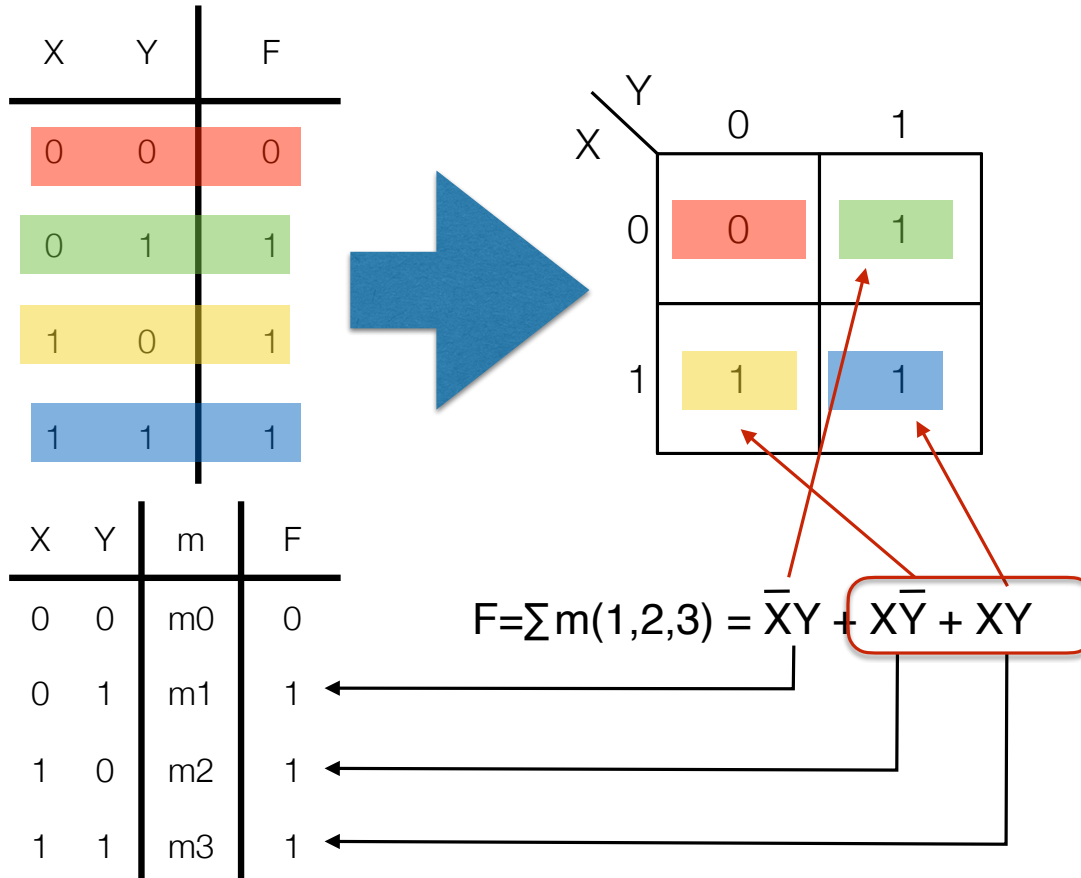
# Karnaugh maps express functions

- Fill out table with value of a function




# Karnaugh maps express functions

- Fill out table with value of a function

$$X\bar{Y} + XY = X$$

To simplify, when both midterms  $X\bar{Y}$  and  $XY$  evaluate to 1, they can be “replaced” in the expression by  $X$

X	Y	m	F
0	0	m0	0
0	1	m1	1
1	0	m2	1
1	1	m3	1

 

$$F = \sum m(1,2,3) = \bar{X}Y + X\bar{Y} + XY$$



# Simplification using a k-map

- Whenever two squares share an edge and both are 1, those two terms can be combined to form a single term with one less variable

		Y	
		0	1
X	0	0	1
	1	1	1

$$F = \bar{X}Y + X\bar{Y} + XY$$

		Y	
		0	1
X	0	0	1
	1	1	1

$$F = X + \bar{X}Y$$

(combined  $X\bar{Y} + XY = X$ )

		Y	
		0	1
X	0	0	1
	1	1	1

$$F = Y + X\bar{Y}$$

(combined  $\bar{X}Y + XY = Y$ )

		Y	
		0	1
X	0	0	1
	1	1	1

$$F = X + Y$$

(combined  $X\bar{Y} + XY = X$  and  $\bar{X}Y + XY = Y$ )

# Simplification using a k-map

- Whenever two squares share an edge and both are 1, those two terms can be combined to form a single term with one less variable

		Y	
		0	1
X	0	0	1
	1	1	1

$$F = \bar{X}Y + X\bar{Y} + XY$$

		Y	
		0	1
X	0	0	1
	1	1	1

$$F = X + \bar{X}Y$$

(combined  $X\bar{Y} + XY = X$ )

		Y	
		0	1
X	0	0	1
	1	1	1

$$F = Y + X\bar{Y}$$

(combined  $\bar{X}Y + XY = Y$ )

		Y	
		0	1
X	0	0	1
	1	1	1

$$F = X + Y$$


(combined  $X\bar{Y} + XY = X$  and  $\bar{X}Y + XY = Y$ )

(=  $X\bar{Y} + XY + \bar{X}Y + XY$ ): XY term “repeated” to obtain simplified form
 
## Simplification using a k-map (2)

---

- “Circle” contiguous squares of 1s (# of squares covered must be a power of 2)
- There is a correspondence between circles on a k-map and terms in a function expression
- The bigger the circle, the simpler the term
- Add circles (and terms) until all 1s on the k-map are circled



$$F = X + Y$$

# 3-variable Karnaugh maps

- Use gray ordering on edges with multiple variables
- Gray encoding: order of values such that only one bit changes at a time
- Two minterms are considered adjacent if they differ in only one variable (this means maps “wrap”)

		Y Z			
		X	0 0	0 1	1 1
X	0	m0 $\overline{X}\overline{Y}\overline{Z}$	m1 $\overline{X}\overline{Y}Z$	m3 $\overline{X}YZ$	m2 $\overline{X}Y\overline{Z}$
	X=1 1	m4 $X\overline{Y}\overline{Z}$	m5 $X\overline{Y}Z$	m7 $XYZ$	m6 $XY\overline{Z}$

Or just

**X**

# 3-variable Karnaugh maps

- Use gray ordering on edges with multiple variables
- Gray encoding: order of values such that only one bit changes at a time
- Two minterms are considered adjacent if they differ in only one variable (this means maps “wrap”)

		Y Z			
X		0 0	0 1	1 1	1 0
	X=0 0	m0 $\bar{X}\bar{Y}\bar{Z}$	m1 $\bar{X}\bar{Y}Z$	m3 $\bar{X}YZ$	m2 $\bar{X}Y\bar{Z}$
	1	m4 $X\bar{Y}\bar{Z}$	m5 $X\bar{Y}Z$	m7 $XYZ$	m6 $XY\bar{Z}$

Or just

$\bar{X}$

# 3-variable Karnaugh maps

- Use gray ordering on edges with multiple variables
- Gray encoding: order of values such that only one bit changes at a time
- Two minterms are considered adjacent if they differ in only one variable (this means maps “wrap”)

		Y Z			
		0 0	0 1	1 1	1 0
X	0	m0 $\bar{X}\bar{Y}\bar{Z}$	m1 $\bar{X}\bar{Y}Z$	m3 $\bar{X}YZ$	m2 $\bar{X}Y\bar{Z}$
	1	m4 $X\bar{Y}\bar{Z}$	m5 $X\bar{Y}Z$	m7 $XYZ$	m6 $XY\bar{Z}$

Or just

**Y**

# 3-variable Karnaugh maps

- Use gray ordering on edges with multiple variables
- Gray encoding: order of values such that only one bit changes at a time
- Two minterms are considered adjacent if they differ in only one variable (this means maps “wrap”)

Y Z

X

Y=0


	0 0	0 1	1 1	1 0
0	m0 $\bar{X}\bar{Y}\bar{Z}$	m1 $\bar{X}\bar{Y}Z$	m3 $\bar{X}YZ$	m2 $\bar{X}Y\bar{Z}$
1	m4 $X\bar{Y}\bar{Z}$	m5 $X\bar{Y}Z$	m7 $XYZ$	m6 $XY\bar{Z}$

Or just

$\bar{Y}$
 
# 3-variable Karnaugh maps

- Use gray ordering on edges with multiple variables
- Gray encoding: order of values such that only one bit changes at a time
- Two minterms are considered adjacent if they differ in only one variable (this means maps “wrap”)




Or just

**Z**


 
# 3-variable Karnaugh maps

- Use gray ordering on edges with multiple variables
- Gray encoding: order of values such that only one bit changes at a time
- Two minterms are considered adjacent if they differ in only one variable (this means maps “wrap”)




Or just

$\bar{Z}$
 
# 3-variable Karnaugh maps

- Use gray ordering on edges with multiple variables
- Gray encoding: order of values such that only one bit changes at a time
- Two minterms are considered adjacent if they differ in only one variable (this means maps “wrap”)




X=1 and Z=0

Or just

$X\bar{Z}$



# 4-variable Karnaugh maps

- Extension of 3-variable maps

 


Product terms are just  $2^i \times 2^j$  boxes (that might wrap around)

  - A **product term**, which, viewed in a K-Map is a  $2^i \times 2^j$  size “rectangle” (possibly wrapping around) where  $i=0,1,2, j=0,1,2$



Product terms are just  $2^i \times 2^j$  boxes (that might wrap around)

 
- A **product term**, which, viewed in a K-Map is a  $2^i \times 2^j$  size “rectangle” (possibly wrapping around) where  $i=0,1,2, j=0,1,2$



Note: bigger rectangles = fewer literals


# 4-variable Karnaugh maps example

W	X	Y	Z	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

 

# 4-variable Karnaugh maps example

W	X	Y	Z	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

 


K-maps make F expressed as SoP easy to see, e.g.,

$$\bar{Y} + \bar{W}Y\bar{Z} + W\bar{X}Y\bar{Z}$$

Can the expression for F be simplified further?

# 4-variable Karnaugh maps example

W	X	Y	Z	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

 

$$\bar{Y} + \bar{W}\bar{Z} + \bar{X}\bar{Z}$$

Rule when picking product terms: Must cover only 1's, but OK to overlap. Bigger rectangles are better (fewer literals)



# Implicant terminology for a function $F$


---

- Given a function  $F$ :
  - An **implicant** is a product term (i.e., a “box” whose dimensions are powers of 2) comprised of minterms for which the function  $F$  evaluates to 1
    - i.e., the “box” must only cover squares that are 1
  - **prime implicant**: An implicant not contained within another implicant (remember that implicant dimensions must be powers of 2!)
  - **essential prime implicant**: a **prime implicant** that is the **only prime implicant** to cover some minterm.
 
## 4-variable Karnaugh maps (3)


---

- List all of the prime implicants for this function
- Is any of them an essential prime implicant?
- What is a simplified expression for this function?



 
## 4-variable Karnaugh maps (3)

- List all of the prime implicants for this function
- Is any of them an essential prime implicant?
- What is a simplified expression for this function?



 
# 4-variable Karnaugh maps (3)

- List all of the prime implicants for this function
- Is any of them an essential prime implicant?
- What is a simplified expression for this function?


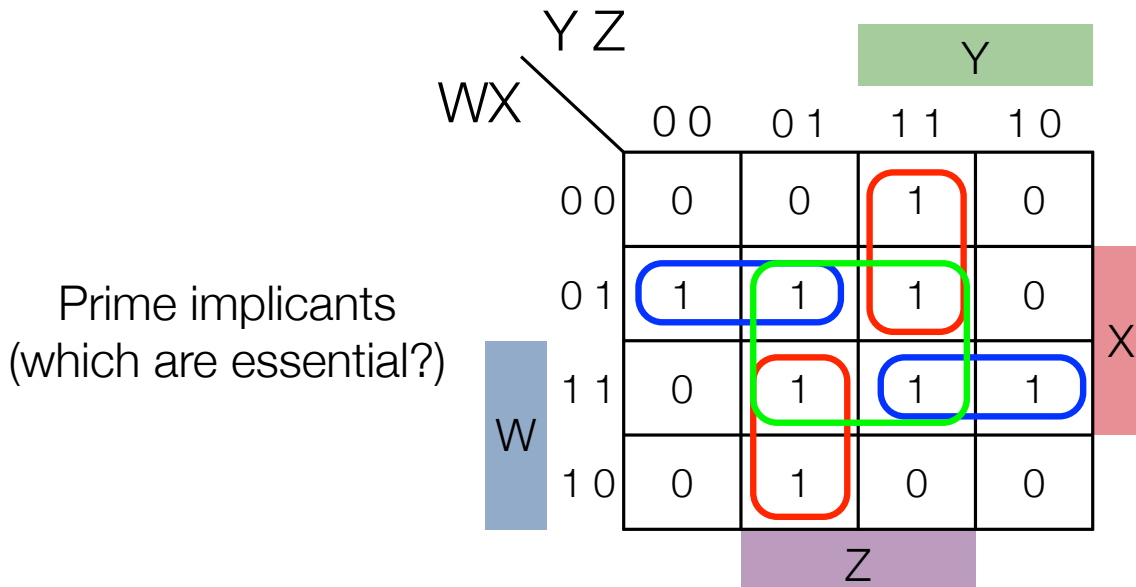
## 4-variable Karnaugh maps (3)

- List all of the prime implicants for this function
- Is any of them an essential prime implicant?
- What is a simplified expression for this function?




## 4-variable Karnaugh maps (3)

- List all of the prime implicants for this function
- Is any of them an essential prime implicant?
- What is a simplified expression for this function?

**The blue and red are essential:** each has 1 minterm not covered by any other prime implicant

 **Green not essential:** every covered minterm also covered by blue or red prime implicant



# Using K-maps to build simplified circuits

---

- Step 1: Identify all PIs and essential PIs
- Step 2: Include all Essential PIs in the circuit (Why?)
- Step 3: If any 1-valued minterms are uncovered by EPIs, choose PIs that are “big” and do a good job covering
  - **Selection Rule:** a heuristic for usually choosing “good” PIs: choose the PIs that minimize overlap with one another and with EPIs


1	1	1	0
0	1	1	0
1	1	1	1
1	1	0	1

1	1	0	0
0	1	1	0
0	0	1	1
1	0	0	1
 
# Using K-maps to build simplified circuits


- Step 1: Identify all PIs and essential PIs
- Step 2: Include all Essential PIs in the circuit (Why?)
- Step 3: If any 1-valued minterms are uncovered by EPIs, choose PIs that are “big” and do a good job covering
- **Selection Rule:** a heuristic for usually choosing “good” PIs: choose the PIs that minimize overlap with one another and with EPIs

Red bounds are EPIs (solo-covered minterm shown in red)



Also need  
(purple or blue) and  
(yellow or green)

All blue PIs or all  
green PIs cover

 



# Design example : 2-bit multiplier

---

a <sub>1</sub>	a <sub>0</sub>	b <sub>1</sub>	b <sub>0</sub>	z <sub>3</sub>	z <sub>2</sub>	z <sub>1</sub>	z <sub>0</sub>
0	0	0	0				
0	0	0	1				
0	0	1	0				
0	0	1	1				
0	1	0	0				
0	1	0	1				
0	1	1	0				
0	1	1	1				
1	0	0	0				
1	0	0	1				
1	0	1	0				
1	0	1	1				
1	1	0	0				
1	1	0	1				
1	1	1	0				
1	1	1	1				

two 2-bit #'s multiplied together to give a 4-bit solution

e.g.,  $a_1a_0 = 10$ ,  $b_1b_0 = 11$ ,  $z_3z_2z_1z_0 = 0110$

## Design example : 2-bit multiplier (SOLUTION)

---

a1	a0	b1	b0	z3	z2	z1	z0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

# Design example : 2-bit multiplier (SOLUTION)

a1	a0	b1	b0	z3	z2	z1	z0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

				b <sub>0</sub>
	0	0	0	0
	0	0	0	0
a <sub>1</sub>	0	0	1	0
	0	0	0	0
				b <sub>1</sub>

$$z_3 = a_1 a_0 b_1 b_0$$

$$z_1 = (\text{exercise})$$

				b <sub>0</sub>
	0	0	0	0
	0	0	1	1
a <sub>1</sub>	0	1	0	1
	0	1	1	0
				b <sub>1</sub>

				b <sub>0</sub>
	0	0	0	0
	0	0	0	0
a <sub>1</sub>	0	0	0	1
	0	0	1	1
				b <sub>1</sub>

$$z_2 = a_1 \bar{a}_0 b_1 + a_1 b_1 \bar{b}_0$$

$$z_0 = a_0 b_0$$


				b <sub>0</sub>
	0	0	0	0
	0	1	1	0
a <sub>1</sub>	0	1	1	0
	0	0	0	0
				b <sub>1</sub>

K-Maps: Complements, PoS, don't care conditions


---
 
# Finding $\bar{F}$

- Find prime implicants corresponding to the 0s on a k-map


 
$$F = \bar{Y} + \bar{X}\bar{Z} + \bar{W}\bar{Z}$$



$$\bar{F} = YZ + WXY$$

# PoS expressions from a k-map

- Find  $\bar{F}$  as SoP and then apply DeMorgan's
- or: Cover the boxes with all "0"s - the sum term "0's out" that box

Y Z					
		0 0	0 1	1 1	1 0
W X	0 0	1	1	0	1
	0 1	1	0	0	0
	1 1	1	0	0	0
	1 0	1	1	0	1

$$\bar{F} = YZ + XZ + YX$$

DeMorgan's

$$F = (\bar{Y} + \bar{Z})(\bar{Z} + \bar{X})(\bar{Y} + \bar{X})$$

**Don't Care Conditions**

# Don't care conditions

- There are circumstances in which the value of an output doesn't matter
- For example, in that 2-bit multiplier, what we
- are told neither a nor b will be input as 0
  - “don't care” what the output looks like for the input cases that will not occur
- Don't care situations are denoted by an “X” in a truth table and in Karnaugh maps.
- Can also be expressed in minterm form:

$$z2 = \sum m(10,11,14)$$

$$d2 = \sum m(0,1,2,3,4,8,12)$$

a1	a0	b1	b0	z3	z2	z1	z0
0	0	0	0	X	X	X	X
0	0	0	1	X	X	X	X
0	0	1	0	X	X	X	X
0	0	1	1	X	X	X	X
0	1	0	0	X	X	X	X
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	X	X	X	X
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	X	X	X	X
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1



# Simple Don't Care Example

---

- Let  $F = AB + \overline{A}\overline{B}$
- Suppose we know the input combo  $A=1, B=0$  will never occur
- Can we replace  $F$  with a simpler function  $G$  whose output matches for all inputs we do care about?
- Let  $H$  be the function with Don't-care conditions for obsolete inputs

A	B	F
0	0	1
0	1	0
1	0	0
1	1	1

# Simple Don't Care Example

- Let  $F = AB + \overline{A}\overline{B}$
- Suppose we know the input combo  $A=1, B=0$  will never occur
- Can we replace  $F$  with a simpler function  $G$  whose output matches for all inputs we do care about?

A	B	F
0	0	1
0	1	0
1	0	0
1	1	1

Inputs will  
not occur

Since  $A=1, B=0$  will not occur,  
don't care what circuit  
produces for  $A=1, B=0$  inputs

# Simple Don't Care Example

---

- Let  $F = AB + \overline{A}\overline{B}$
- Suppose we know the input combo  $A=1, B=0$  will never occur
- Can we replace  $F$  with a simpler function  $G$  whose output matches for all inputs we do care about?
- Let  $H$  be the function with Don't-care conditions for obsolete inputs

A	B	F	H
0	0	1	1
0	1	0	0
1	0	0	X
1	1	1	1

Inputs will  
not occur →

# Simple Don't Care Example

---

- Let  $F = AB + \overline{A}\overline{B}$
- Suppose we know the input combo  $A=1, B=0$  will never occur
- Can we replace  $F$  with a simpler function  $G$  whose output matches for all inputs we do care about?
- Let  $H$  be the function with Don't-care conditions for obsolete inputs

A	B	F	H	G
0	0	1	1	1
0	1	0	0	0
1	0	0	X	1
1	1	1	1	1

Inputs will  
not occur →

# Simple Don't Care Example

---

- Let  $F = AB + \overline{A}\overline{B}$
- Suppose we know the input combo  $A=1, B=0$  will never occur
- Can we replace  $F$  with a simpler function  $G$  whose output matches for all inputs we do care about?
- Let  $H$  be the function with Don't-care conditions for obsolete inputs

Inputs will  
not occur →

A	B	F	H	G
0	0	1	1	1
0	1	0	0	0
1	0	0	X	1
1	1	1	1	1

- Both  $F$  &  $G$  are appropriate functions for  $H$

# Simple Don't Care Example

- Let  $F = AB + \overline{A}\overline{B}$
- Suppose we know the input combo  $A=1, B=0$  will never occur
- Can we replace  $F$  with a simpler function  $G$  whose output matches for all inputs we do care about?
- Let  $H$  be the function with Don't-care conditions for obsolete inputs

Inputs will  
not occur

A	B	F	H	G
0	0	1	1	1
0	1	0	0	0
1	0	0	X	1
1	1	1	1	1

- Both  $F$  &  $G$  are appropriate functions for  $H$

$$G = AB + \overline{B}$$

- $G$  is (slightly) simpler than  $F$  (3 instead of 4 literals), and gets the job done!

## 2-bit multiplier non-0 multiplier (SOLUTION)

a1	a0	b1	b0	z3	z2	z1	z0
0	0	0	0	X	X	X	X
0	0	0	1	X	X	X	X
0	0	1	0	X	X	X	X
0	0	1	1	X	X	X	X
0	1	0	0	X	X	X	X
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	X	X	X	X
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	X	X	X	X
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

			b <sub>0</sub>	
	X	X	X	X
	X	0	0	0
a <sub>1</sub>	X	0	1	0
	X	0	0	0
			b <sub>1</sub>	

$$z_3 = a_1 a_0 b_1 b_0$$

			b <sub>0</sub>	
	X	X	X	X
	X	0	0	0
a <sub>1</sub>	X	0	0	1
	X	0	1	1
			b <sub>1</sub>	

$$z_2 = a_1 \bar{b}_0 + \bar{a}_0 b_1$$

$$(\text{vs. } a_1 \bar{a}_0 b_1 + a_1 b_1 \bar{b}_0)$$

Revised rule for “implicant”:

1's must be covered

0's must not be covered

X's are optionally covered



## 2-bit multiplier non-0 multiplier (SOLUTION)

a1	a0	b1	b0	z3	z2	z1	z0
0	0	0	0	X	X	X	X
0	0	0	1	X	X	X	X
0	0	1	0	X	X	X	X
0	0	1	1	X	X	X	X
0	1	0	0	X	X	X	X
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	X	X	X	X
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	X	X	X	X
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

Still have prime and essential prime implicants

$z_1 = (\text{exercise})$

$z_0 = a_0 b_0$

  

All above prime implicants are essential



# Final thoughts on Don't care conditions

---

- Sometimes “don't cares” greatly simplify circuitry

				D									
				1	X	X	X						
				X	1	X	X						
A					0	0	1	X	B				
					0	0	X	1					
								C					

$$\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + ABCD + A\bar{B}C\bar{D} \text{ vs. } \bar{A} + C$$

# High-level Summary

---

- **minterm** (of  $k$  variables): a product term formed from the literals of each variable (exist without function)
- A **function** (e.g., for  $F = A + \bar{A}BC$ ) can be constructed by ORing (summing) together the minterms for which the function = 1
- **implicant (of a function)**: a product term (of literals) that is “contained” within the function (formed from minterms where the function = 1)
- **prime implicant**: a product term which, if any literal is remove, is no longer “contained” within the function
- **essential prime implicant**: when a function is expressed as an OR (sum) of prime implicants, this one must be included.

$$AB\bar{C}$$

$$ABC + AB\bar{C} + \bar{A}BC + \bar{A}\bar{B}\bar{C} + \bar{A}BC$$

$$AB$$