

3827 OH

Eumin Hong (eh2890)

Columbia University

February 8, 2022

Overview

1 Announcements

- Upcoming Assessments
- Poll Results
- Feedback Form

2 Notable Concepts

- 2's Complement Overflow Logic
- SoP, PoS
- Minterms and Maxterms
- Minterms, Maxterms, and K-maps
- Converting SoP to PoS
- Simplifying with K-Maps

- Recognizing XOR in K-Maps
- XOR in K-Maps Example
- Multi-Wire Notation
- Combinational Circuits
- Decoder/MUX Notation

3 Homework 2

- Problem 1
- Problem 2
- Problem 3
- Problem 4
- Problem 5
- Problem 6
- Problem 7
- Problem 8

Announcements

Announcements: Upcoming Assessments

- HW2 is due on Friday 2/11
- HW3 is due on Friday 2/18
- HW4 is due on Friday 2/25
- Homework is due at 11:59 pm (follow Gradescope time for deadline)

Announcements: Poll Results

- Online OH (except MIPS): 80%
- Email only: 62.5%
- Will create Slack for those who would like to join; will check frequently

Announcements: Feedback Form

- Form: <https://forms.gle/cnUmKVNYN7WvRbHA6>

Notable Concepts

Notable Concepts: 2's Complement Overflow Logic

- Why can you just check the last two carries to detect overflow in 2's complement?
- Let P be a positive number and N be a positive number. Consider the cases where the carries are different (implying overflow; carries are left to right):

→ ① $P + P$: if carries are 0 and 1, then result is negative


② $N + N$: if carries are 1 and 0, then result is positive

③ $P + N$: if carries are 0 and 1, then result is positive

- To see that the result should be positive, compare P and N
- Let A be P without the MSB and B be N without MSB
- In order for the second carry to be 1, $A > B$ (unsigned comparison), so $A < \bar{B}$
- We consider \bar{B} since we are actually comparing $|P|$ and $|N|$, and so $|P| < |N|$ and output should be negative

④ $P + N$: if carries are 1 and 0, then result is negative (same logic as above)

11110 Negative

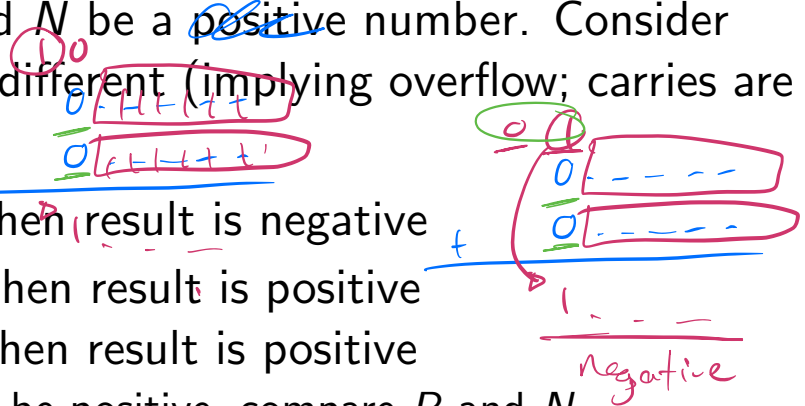

Notable Concepts: SoP, PoS

- Sum of Products: OR of product terms; e.g. $F = \bar{Y} + \bar{X}Y\bar{Z} + XY$
Handwritten notes: "6 literals" above $\bar{X}Y\bar{Z}$, "literal" with an arrow pointing to XY .
- Product of Sums: AND of sum terms; e.g.
 $F = X(\bar{Y} + Z)(X + Y + \bar{Z})$
Handwritten note: "wrt literals" with an arrow pointing to the expression.
- SoP and PoS are not the simplest form, just a canonical form
 - E.g. $F = X \oplus Y$ is simpler than $F_{\text{SoP}} = X\bar{Y} + \bar{X}Y$ and $F_{\text{PoS}} = (X + Y)(\bar{X} + \bar{Y})$
Handwritten notes: Underlines under $X\bar{Y}$, $\bar{X}Y$, and $(X + Y)(\bar{X} + \bar{Y})$.

Notable Concepts: Minterms and Maxterms



- Minterm: product term with all variables appearing exactly once (either complemented or not); e.g. $\bar{A}BC\bar{D}$
 - Evaluates to 1 for exactly one variable assignment combination, 0 otherwise
- Maxterm: sum term with all variables appearing exactly once (either complemented or not); e.g. $A + \bar{B} + \bar{C} + D$
 - Evaluates to 0 for exactly one variable assignment combination, 1 otherwise

$$\begin{aligned} A &= 0 \\ B &= 1 \\ C &= 1 \\ D &= 0 \end{aligned}$$

$$\begin{aligned} A &= 0 \\ B &= 1 \\ C &= 1 \\ D &= 0 \end{aligned}$$

Notable Concepts: Minterms, Maxterms, and K-maps

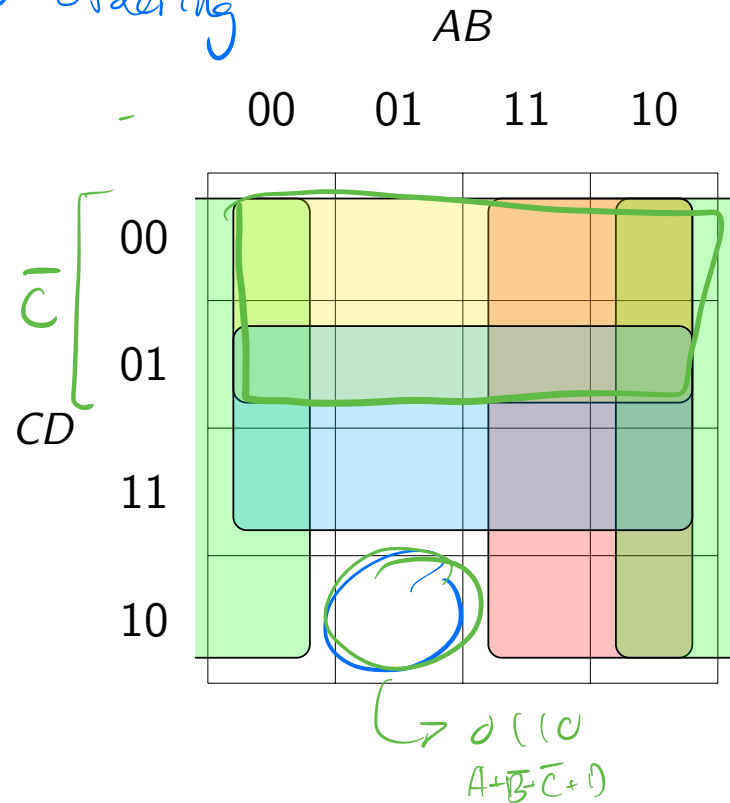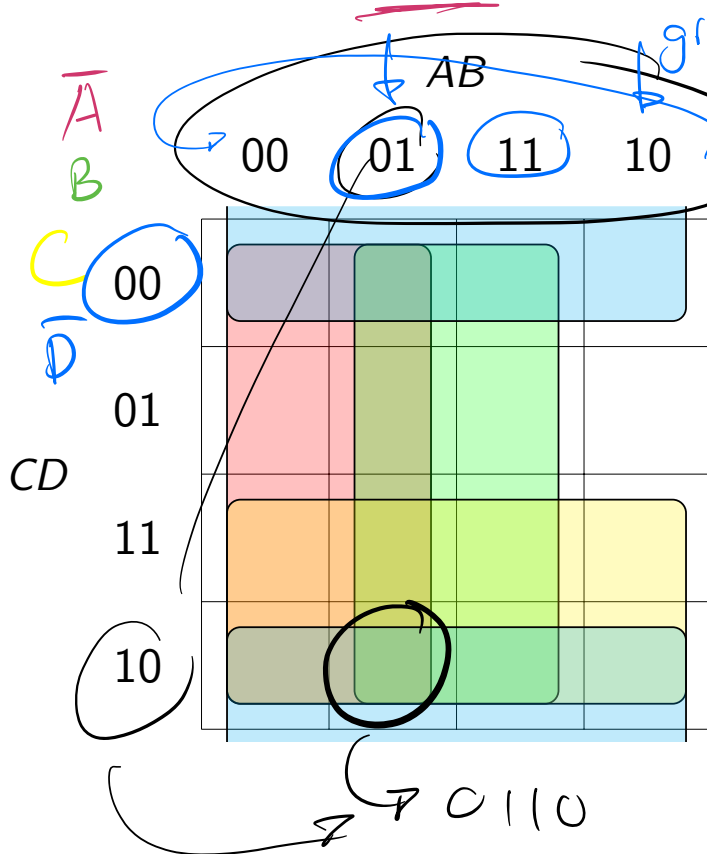- How do minterms and maxterms relate to K-maps?
- For minterm $\bar{A}BC\bar{D}$ (left) and maxterm $A + \bar{B} + \bar{C} + D$ (right):




Notable Concepts: Converting SoP to PoS

- 1 Compute \bar{F} : swap AND and OR operations, flip literals
- 2 Convert \bar{F} to SoP form
- 3 Compute $\bar{\bar{F}} = F$: swap AND and OR operations, flip literals
 - Complemented F twice
 - Complementing F is SoP form gets \bar{F} in PoS form
 - Example: converting $F = \bar{A}\bar{C} + \bar{B}$ into PoS form

$$\bar{\bar{X}} = X$$



- 1 $\bar{F} = (A + C)B$
- 2 $\bar{F} = AB + BC$ (PoS)
- 3 $\bar{F} = F = (\bar{A} + \bar{B})(\bar{B} + \bar{C})$
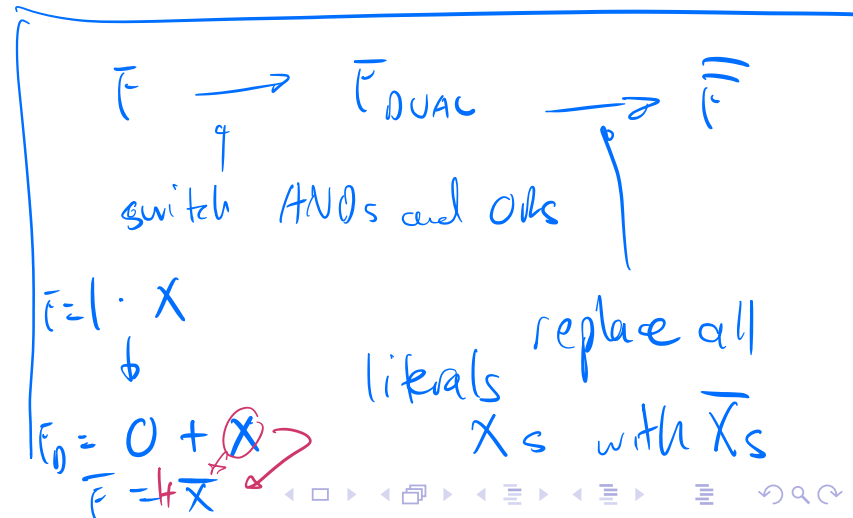
$$(\bar{A} \cdot \bar{C}) \rightarrow \bar{\bar{A}} + \bar{\bar{C}}$$



Notable Concepts: Simplifying with K-Maps

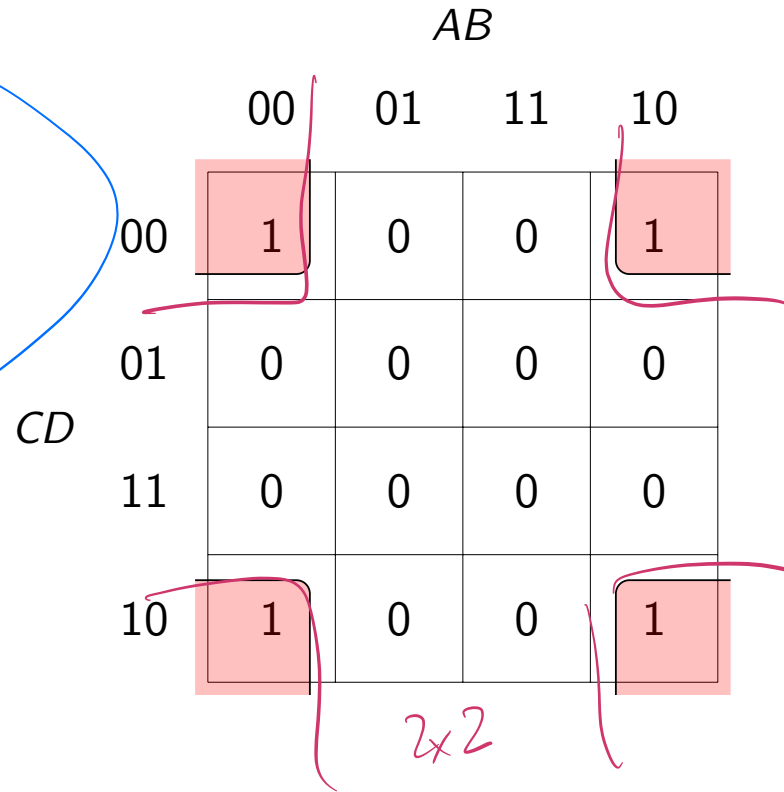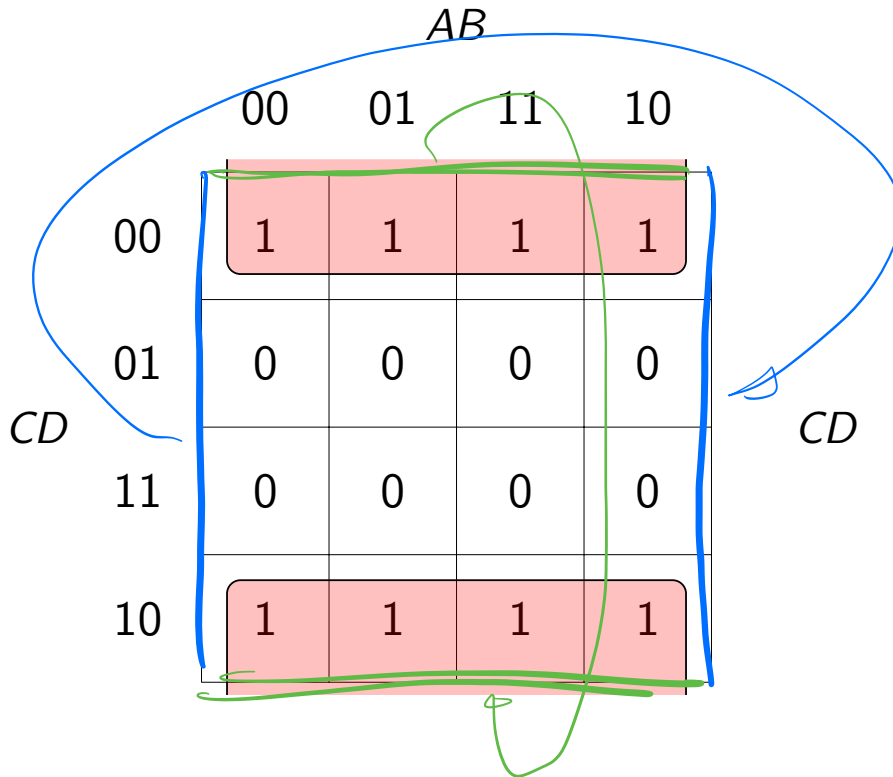- Try to take largest essential prime implicant
- Remember that K-maps are “wrapped around”:



Notable Concepts: Recognizing XOR in K-Maps

- K-maps for $A \oplus B$ (left) and $A \oplus B \oplus C$ (right):

		A	
		0	1
B	0	0	1
	1	1	0

		AB			
		00	01	11	10
C	0	0	1	0	1
	1	1	0	1	0

Description

Truth table \rightarrow K-map \rightarrow Boolean expression \rightarrow Circuit

- Note the checkered pattern
- Minterms/maxterms have more literals than the XOR operations

Notable Concepts: XOR in K-Maps Example

	AB			
	00	01	11	10
00	1	0	1	0
01	0	0	0	0
11	0	0	0	0
10	0	1	0	1

- Note that the middle two rows (D) are all 0

- complements
- The final expression is of the form $F = \overline{D}(F')$ where F' is mostly XORs

- Remove middle two rows:

$D = 1$


	AB			
	00	01	11	10
0	1	0	1	0
1	0	1	0	1

000 110 011 101


- complement
- $F = \overline{D}(A \oplus B \oplus C)$

Notable Concepts: Multi-Wire Notation

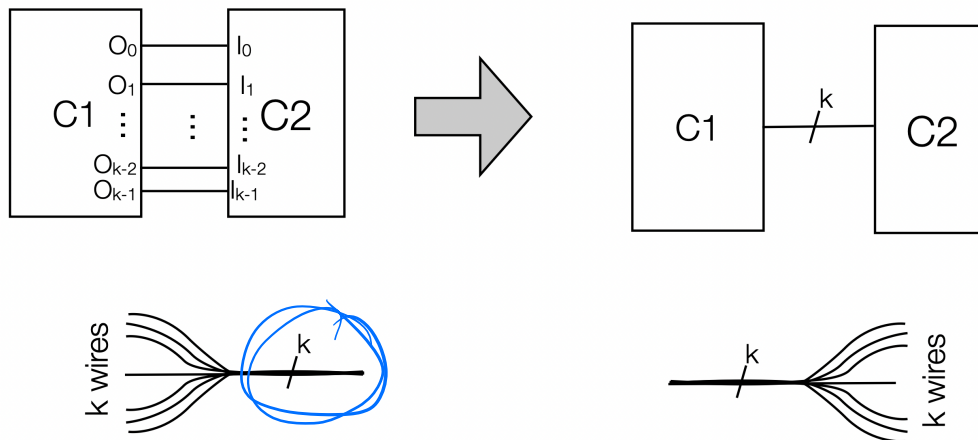

- Can have multiple wires in parallel (from 3827_Lecture_04.pdf, slide 30):



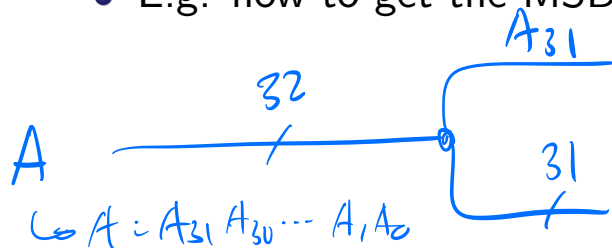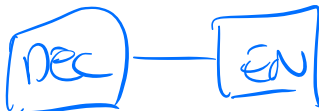- But remember: these are just wires
 - E.g. how to get the MSB of a k -bit number represented by k wires?



Notable Concepts: Combinational Circuits



- Enabler: for “turning on/off” ^{outputs} ~~inputs~~
 - High-level circuit for other circuits, “enable” functionality can be added with an input labelled “E”
- Decoder: set one of 2^k outputs to 1 (others are 0) based on unsigned binary representation of k -bit input
- Multiplexer (MUX): pass one of 2^k inputs as output based on k -bit “selector” input 

$ABC \rightarrow BC A$
 $BC 0$
 $BC 1$
- Shifter: shifts bits of k -bit input
 - Can have input to control how much bits are shifted by, or can be hardcoded
- Adders (unsigned, 2's complement): half/full adders can make ripple carry adder
 - Carry lookahead also exists (reduced depth with increased parallelism)

Dec (input
↳ size k bits) \mathbb{Z}_σ

Notable Concepts: Decoder/MUX Notation

- Must label everything in your combinational circuits
- Consider the two MUXes:

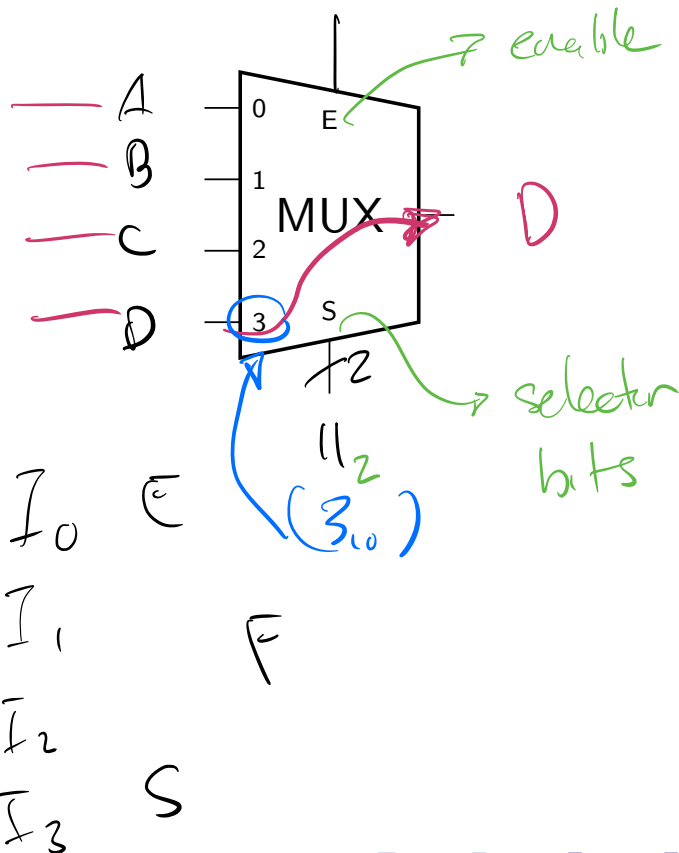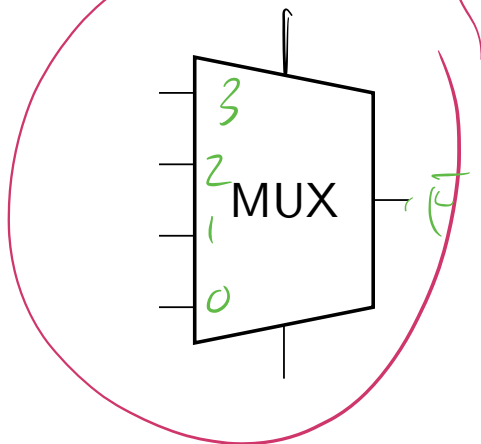

Homework 2

Homework 2: Problem 1

Simplify the following Boolean expressions to a minimum number of literals:

(a) $\overline{B}C + \overline{B}\overline{C}D$

$\overline{B}(C + \overline{C}D)$



(b) $(\overline{Y} + Z)(Y + \overline{Z})$

$C + \overline{C}D$
X f


(c) $\overline{C}\overline{D} + C\overline{D}A + DA$

(d) $X(\overline{C}Y + \overline{C}\overline{Y}) + X(\overline{W}\overline{C} + \overline{W}C)$

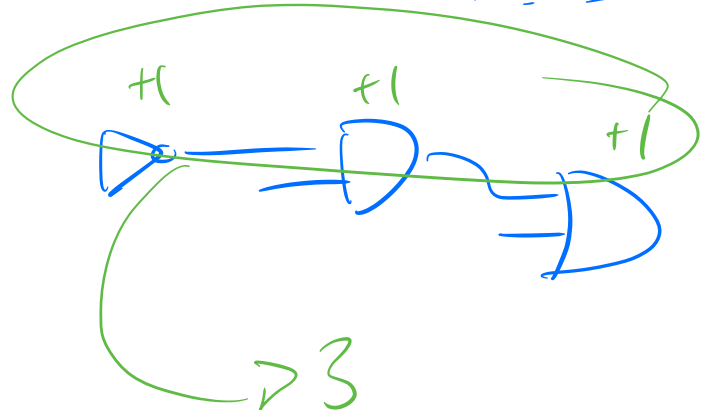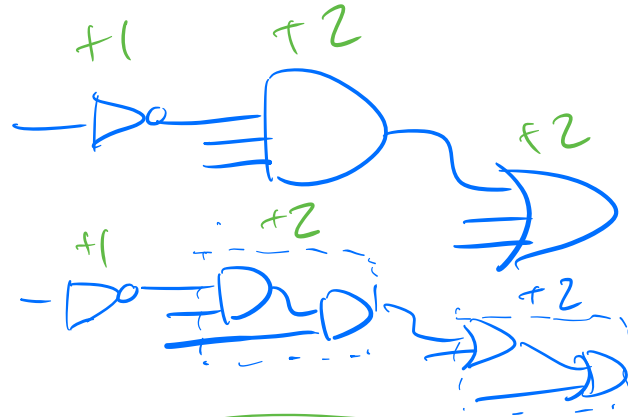(e) $(\overline{B}\overline{C} + BD + \overline{C}D)(\overline{B} + C + \overline{B}C)$



$C + \overline{C}D \rightarrow C + D$

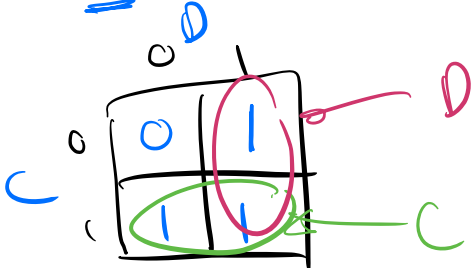

Homework 2: Problem 2

Reduce the following Boolean expressions to the indicated number of literals:

(a) $Y + \bar{Z}(W + \overline{Y + W})$ to two literals

$$Z + ZW \rightarrow (1+W)Z$$

(b) $\bar{Y}X + Y\bar{X}Z + \bar{Y}\bar{X}$ to three literals

(c) $\bar{Y}X(\bar{W} + ZW) + X(Y + \bar{Y}\bar{Z}W)$ to one literal

$$\begin{aligned} & Y + \bar{Z}(W + \bar{W}\bar{Y}) \\ &= Y + \bar{Z}(W + \bar{Y}) \\ &= Y + \bar{Z}W + \bar{Z}\bar{Y} \\ &= Y + \bar{Y}\bar{Z} + \bar{Z}W \\ &= Y + \underbrace{\bar{Z}}_{\bar{Z} \cdot 1} + \underbrace{\bar{Z}W}_{\bar{Z} \cdot 1} \end{aligned}$$

$$\begin{aligned} &= Y + \bar{Z}(1+W) \\ &= Y + \bar{Z} \cdot 1 \\ &= Y + \bar{Z} \end{aligned}$$

$$X = X \cdot 1$$

Homework 2: Problem 3

Using DeMorgan's theorem (as many times as necessary), express the function $F = \bar{X}Z + X\bar{Z}Y + \bar{X}\bar{Y}$ with only:

- (a) OR and complement operations
- (b) AND and complement operations

Homework 2: Problem 4

Find the complement of the following expressions:

(a) $\overline{B}\overline{D} + BD$

(b) $(C + \overline{B}D)(C + \overline{B} + \overline{D})(\overline{C}\overline{B} + \overline{D})$

(c) $\overline{W}\overline{Y}(Z\overline{X} + \overline{Z}X) + WY(Z + X)(\overline{Z} + \overline{X})$

(d) $(\overline{B} + \overline{D})AC + E$

Homework 2: Problem 5

Convert the following into sum-of-products and product-of-sums forms:

a) $(\bar{A} + \bar{B}\bar{D})(\bar{D} + A\bar{C})$

b) $(\bar{Z} + Y)\bar{X}(\bar{X} + Z) + X$

c) $(\bar{Z} + XW + \bar{W}Y)(\bar{X} + \bar{Z}\bar{Y})$

1) SOP

2) POS

Homework 2: Problem 6

Simplify the following boolean expressions using a K-map:

(a) $B\bar{C} + CD + B\bar{D} + \bar{B}\bar{C}D$

(b) $\bar{Y}\bar{Z} + \bar{X}\bar{Z} + ZX\bar{Y}$

(c) $XW + \bar{X}\bar{Z} + X\bar{Z}\bar{W}$

Homework 2: Problem 7

Simplify in Sum-of-product form via a K-map (indicate what you identify as prime implicants and essential prime implicants). Recall that $m(i)$ is the product term whose variables are complemented when and only when their position corresponds to a '0' in the binary representation of i , e.g., $m(5) = \overline{W}X\overline{Y}Z$.

- (a) $F(W, X, Y, Z) = \sum m(0, 4, 5, 7, 9, 12, 13, 14)$
- (b) $F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 8, 9, 10, 11, 13, 15)$
- (c) $F(A, B, C, D) = \sum m(0, 2, 3, 5, 7, 8, 10, 11, 14, 15)$
- (d) $F(W, X, Y, Z) = \sum m(0, 1, 2, 5, 6, 7, 8, 9, 10, 13, 14, 15)$
- (e) $F(W, X, Y, Z) = \sum m(0, 1, 2, 5, 8, 9, 11, 12)$
- (f) $F(A, B, C, D) = \sum m(1, 3, 6, 7, 9, 13, 14, 15)$

0	1	3	2
4	5	7	6
12	13	15	14
8	9	11	10

$WX YZ \rightarrow 10 \ 11 \rightarrow 11_{10} \text{ (in decimal)}$

Yz

	00	01	11	10
00	1	0	0	0
01	1	1	1	0
11	1	1	0	1
10	0	1	0	0

WX

Homework 2: Problem 8

Simplify into Sum-of-product form the following Boolean functions F together with the don't care conditions d :

- (a) $F(W, X, Y, Z) = \sum m(0, 1, 3, 5, 7), d(W, X, Y, Z) = \sum m(2, 4, 6)$
- (b) $F(A, B, C, D) = \sum m(2, 6, 7, 11, 14, 15), d(A, B, C, D) = \sum m(0, 8, 12, 13)$
- (c) $F(A, B, C, D) = \sum m(2, 7, 9, 10, 15), d(A, B, C, D) = \sum m(3, 6, 14)$